
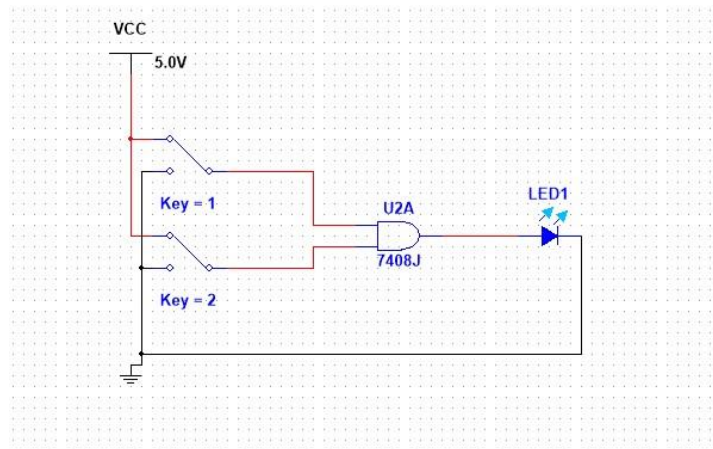


Multisim circuit:


AND-Gate Circuit:

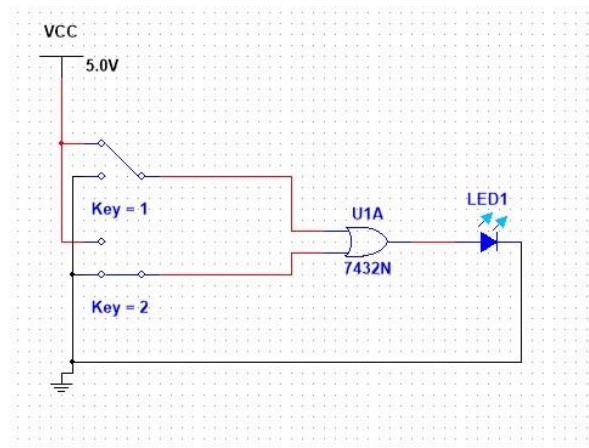

OR-Gate Circuit:




Not-Gate Circuit:

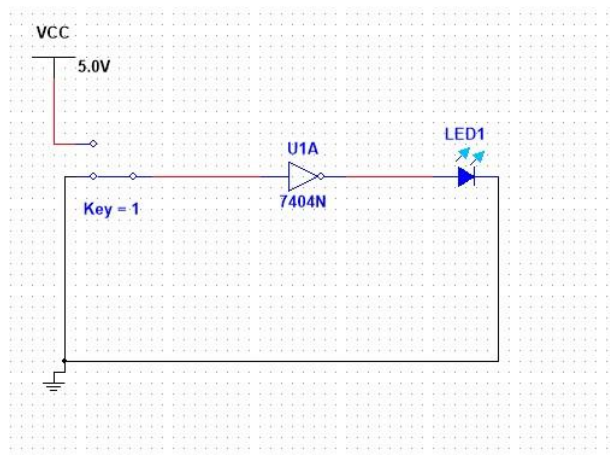


Multisim Circuit:

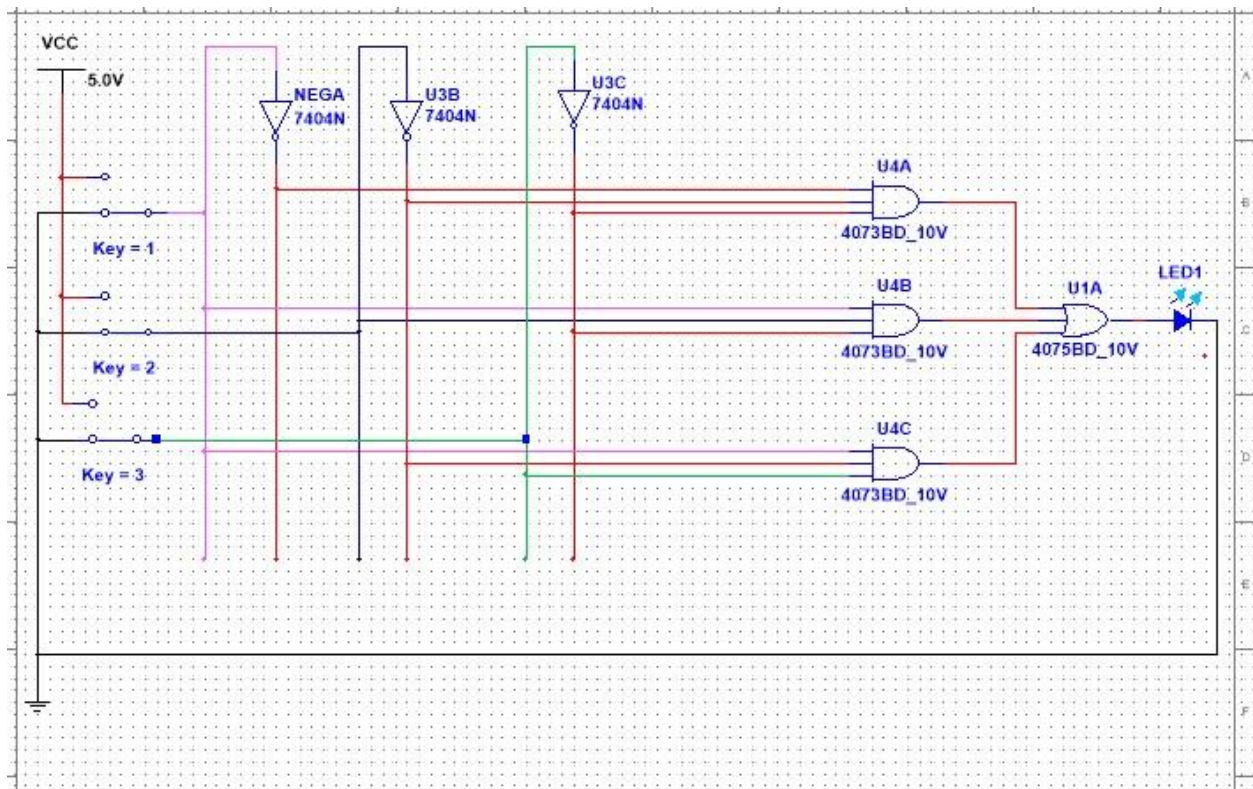Boolean Expression($Y=A'B'C'+AB'C'+AB'C$)




Multisim Circuit:

De-Morgan's Law $(A' \cdot B') = (A+B)'$

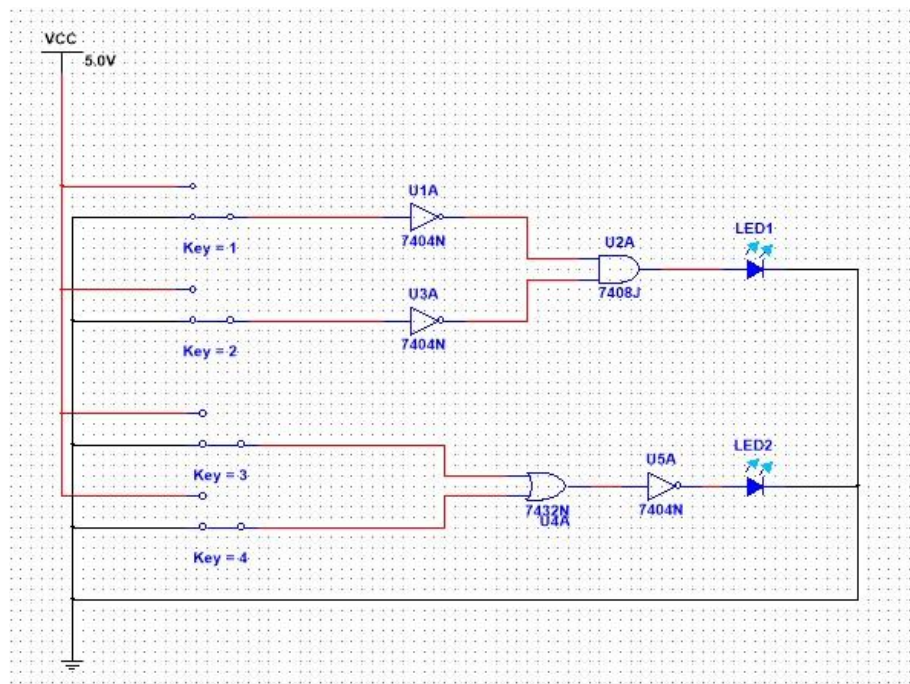


De-Morgan's law $A' + B' = (A \cdot B)'$

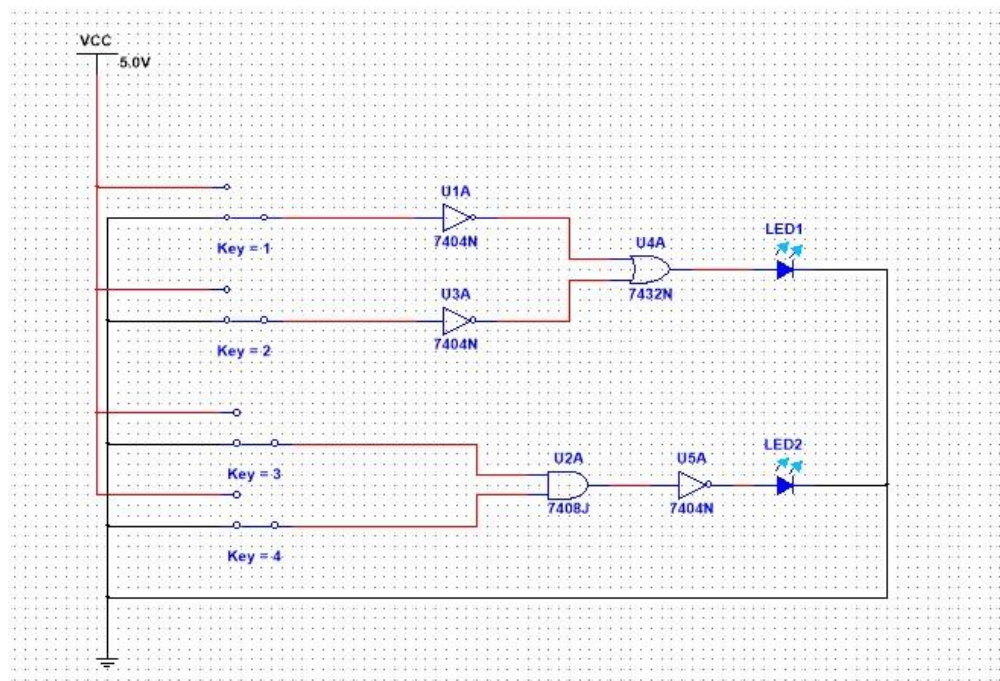


Multisim Circuit:

Multiplexer 2x1:

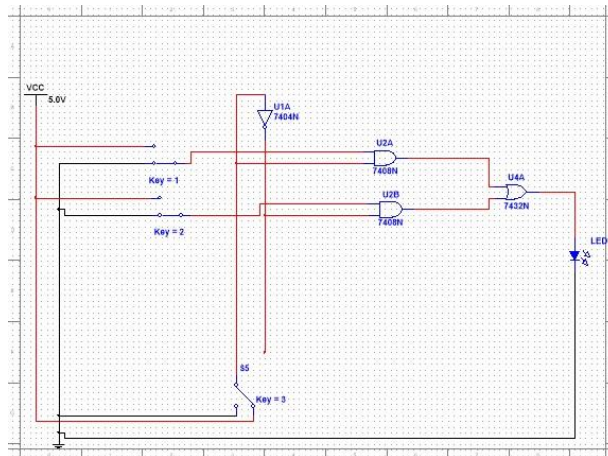

Decoder 2x4(using AND-Gates):

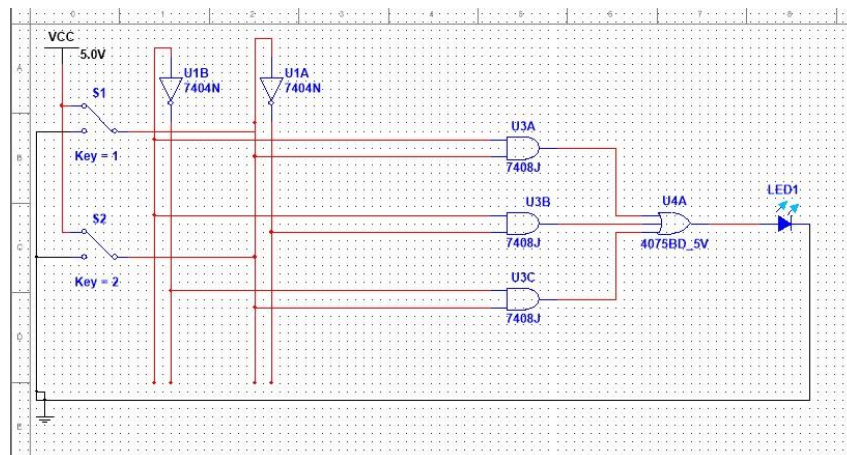

Decoder 2x4(using NAND-Gate):

